Relaxation Oscillator Values and Functions

 $R_1 = 47.75k\Omega, \quad R_2 = 47.47k\Omega$

 R_3 values: $21.75k\Omega$, $6.778k\Omega$, $2.199k\Omega$, $.986k\Omega$ C values: $325\mathrm{nF}$, $45\mathrm{nF}$, $33.19\mathrm{nF}$, $4.5\mathrm{nF}$


Function Used

$$f = \overline{\frac{1}{R_3 C}}, \quad f = \frac{1}{2(\ln 3)R_3 C}$$

Measurement/Measured Data

 $F = \overline{64.9~Hz,\, 1520~Hz,\, 85400~Hz,\, 27200}0~Hz$

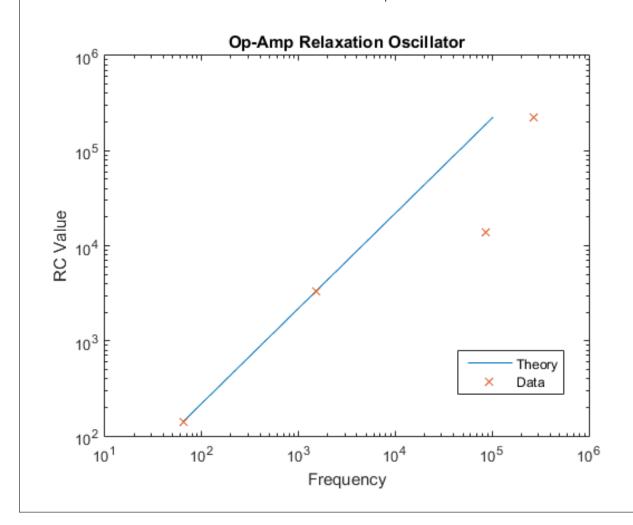Slew Rate: $1.92 \frac{\text{Volts}}{\mu \text{s}}$



555 Timer Values Part 1 $R_1 = .98k\Omega$ R_2 values: $21.75k\Omega$, $6.778k\Omega$, $2.199k\Omega$, $.986k\Omega$ C values: 325nF, 45nF, 33.19nF, 4.5nF 555 Timer Values Part 2 (Duty Cycle) $R_2 = 21.75k\Omega$ R_1 values: $.98k\Omega$, $10k\Omega$, $47.41k\Omega$, $400k\Omega$ C = 3.256 nFFunction Used $f = \frac{1}{R_3C}$, $f = \frac{1.44}{(R_1 + 2R_2)C}$, $DC = \frac{R_1 + R_2}{R_1 + 2R_2}$ Measurement/Measured Data $F = \overline{64.9 \text{ Hz}, 1520 \text{ Hz}, 85400 \text{ Hz}, 27200}0 \text{ Hz}$ DC = 50%, 63%, 81%, 95%555 Timer Oscillator 10⁶ RC Value 10⁴ Theory Data 10² 10¹ 10² 10³ 10⁴ 10⁵ 10⁶ Frequency 100 **Duty Cycle** 80 Theory 60 Data 40 10² 10³ 10⁴ 10⁵ 10⁶ R1 Values

